

Topic 5.2 – Heating effect of electric circuits

Formative Assessment

NAME: _____ TEAM: _____


THIS IS A PRACTICE ASSESSMENT. Show formulas, substitutions, answers (in spaces provided) and units!

A carbon-core resistor consists of a carbon rod having a length of 8.75 mm, a diameter of 0.0250 mm and a resistivity of $3500 \times 10^{-8} \Omega m$.



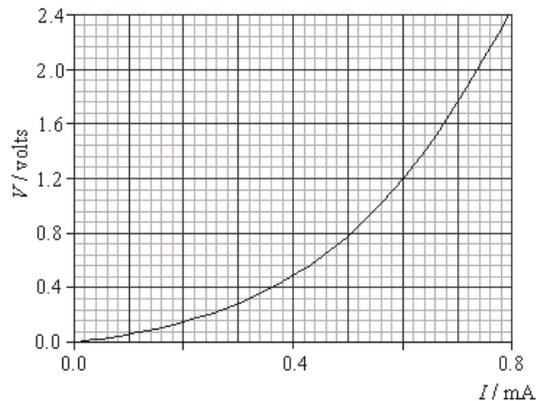1. What is the value of the cross-sectional area of the carbon rod. Be sure your answer is in m^2 .
1. _____
2. What is the resistance of the carbon rod?
2. _____
3. If a current of 1.75 A passes through the resistor, what is the voltage across the resistor?
3. _____

An unknown material has the V-I characteristics shown in the graph.



4. What is the resistance of the material when the current is 0.2 mA? 4. _____
5. What is the resistance of the material when the current is 0.7 mA? 5. _____
6. What is the resistance of the material when the voltage is 1.2 V? 6. _____
7. Is this material ohmic? Explain. _____.

A voltmeter records the displayed potential difference when the leads are placed across a 2200 Ω resistor.



8. What is the current passing through the resistor? 8. _____
9. How much charge passes through the resistor in exactly 1.5 minutes? 9. _____
10. How much electrical energy is required to pass the charge you found in (8) through the resistor? 10. _____
11. What is the fractional error in the voltage measurement? 11. _____

A filament lamp has a rating of 1.50 W. While the bulb is lit, the meter displays the value shown.



12. What is the power dissipation of the lamp? 12. _____
13. What is the current in the lamp? 13. _____
14. What is the resistance of the lamp? 14. _____

A series circuit powered by a 3.0 V cell is shown.


15. What is the total or equivalent resistance of this circuit?
15. _____

16. What is the current through this circuit?

16. _____

17. What are the voltages across each resistor?

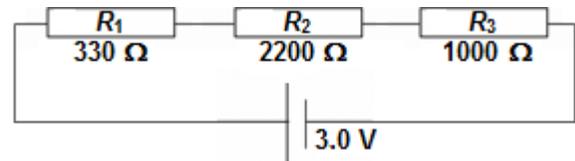17. $V_1 =$ _____
 $V_2 =$ _____
 $V_3 =$ _____



A parallel circuit powered by a 6.0 V cell is shown.

18. What is the total or equivalent resistance of this circuit?
18. _____


19. What is the current through the cell?
19. _____

20. What are the currents through each resistor?

20. $I_1 =$ _____
 $I_2 =$ _____
 $I_3 =$ _____

21. What is the current through the point X?

21. _____

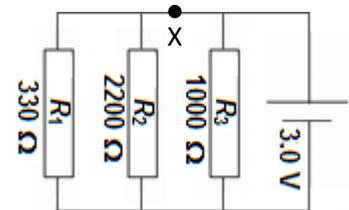

A series circuit powered by a battery whose voltage is 6.0 V is shown in the schematic diagram.

22. Label V_{OUT} and V_{IN} in this circuit.


22. In diagram

23. Suppose the value of R_1 is 2400 Ω. If we would like to “tap” 1.5 V at V_{OUT} what should the value of R_2 be?
23. _____

24. Suppose the value of R_2 is 2400 Ω. If we would like to “tap” 1.5 V at V_{OUT} what should the value of R_1 be?
24. _____

25. What is this type of circuit called?

25. _____

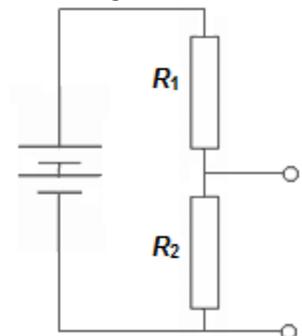


A circuit constructed of resistors and two voltage sources is shown.

26. Use Kirchhoff's rule for I and write the current equations for each junction.
26. _____

27. Use Kirchhoff's rule for V and write the voltage equation for Loop X.
27. _____

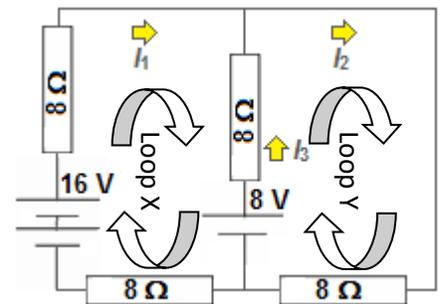28. Use Kirchhoff's rule for V and write the voltage equation for Loop Y.
28. _____



29. Find the values of the three currents and the four resistor voltages. Write them in the diagram.