

EasyEDA Project #3: Police Flashing using 555 Timer

3/30/20

Complete the below schematic design in EasyEDA. Please view the instructional video recording in its entirety before getting started for guidance.

Components needed:

	Quantity
NE555N	1
1K ohms resistor	1
10k ohms resistor	1
100 uF capacitor	1
LED	6
Power Supply 3.7V	1

