

Name: Mr. Lowe

Periods: P7-P9

Date: 3/10/20

EasyEDA Project #1: 555 Timer Flashing LED Circuit Schematic Design

